

## EXPERIMENT: 1

### OBJECTIVE:

Pre determination and verification of ABCD parameters of transmission line.

### THEORY:


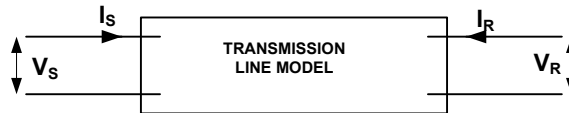
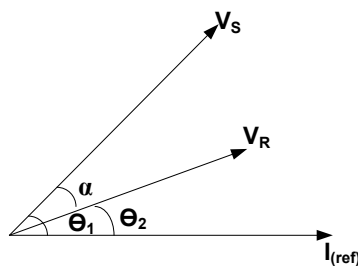


Fig 1(Model of line)

Experimental determination of these parameter can be done by employing voltmeter and ammeters for measurement for their magnitudes and wattmeter suitably used for phase angle measurement.

### PROCEDURE:

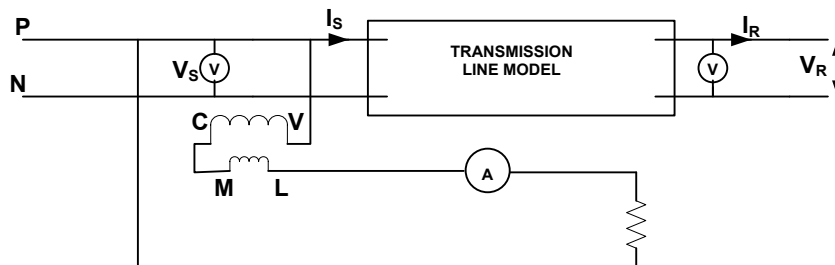

$$P_1 = V_s I \cos \theta_1$$

$$P_2 = V_r I \cos \theta_2$$

$$A = \frac{V_s}{V_r} \quad \text{at } I_r = 0$$

Fig 2 for determining A

**For parameter: A**

- (1) Keeping receiving end voltage open(no load) as shown in fig 2 ,measure  $V_s$ ,  $V_r$ ,  $I$  and power  $P_1$ (when voltage and coil of wattmeter is excited by  $V_s$ )and power  $P_2$ (when voltage coil of wattmeter is excited by  $V_r$ )


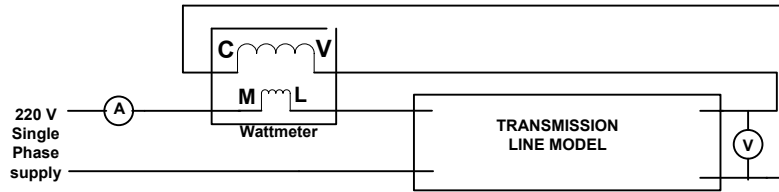


Fig 3 For determining C

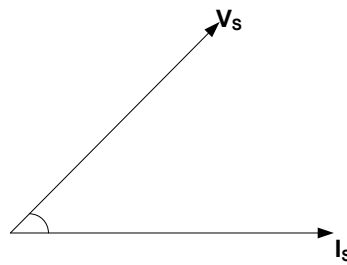

$$C = C \angle \alpha \{ I_s | V_s \} = c \angle \theta \quad (\text{at } I_r = 0)$$

**For parameter: C**

- (2) Connect as show in fig 3, Measure  $V_r, I_s,$  and  $P$ (wattmeter current coil excited by  $I_s,$  and voltage coil excited by  $V_r$ )

Note: Take  $V_r$  as reference phasor & use a low p.f wattmeter.


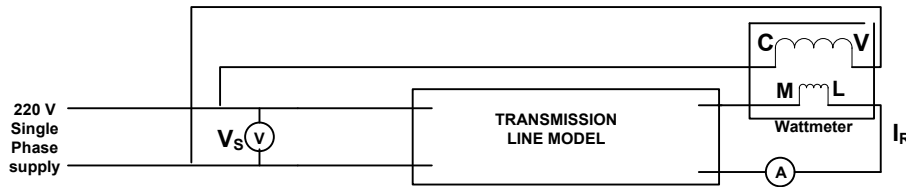


Fig 4 For determining B

$$B = B \angle -\theta$$

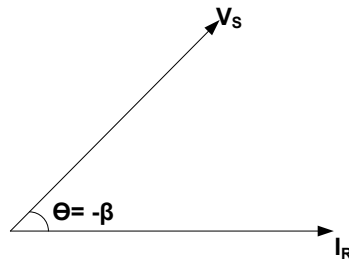

- (3) Short circuit the receiving end side as shown in fig 4. Apply reduced voltage at sending end and try to flow rated  $I_r$ (about 1.0 amps). Measure  $V_s$ ,  $I_r$  and power.


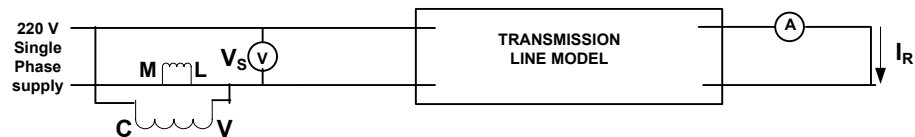


Fig 5 For determining D

$$D = D < -\theta$$

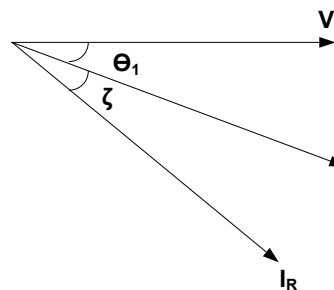

- (4) Connect the circuit as shown in fig 5. Short the receiving end as shown and apply reduced voltage so as to flow approximately 1.0 amps at receiving end. Measure  $I_s$ ,  $I_r$  and  $P_1$  (With voltage coil connected across mains and current coil being excited by  $I_s$ ) and  $P_2$  (With voltage coil connected across mains and current coil being excited by  $I_r$ ). Measure  $P_1$ ,  $P_2$  and  $V$ .

**RESULT:**