

EXPERIMENT: 2

OBJECTIVE:

To measure Positive, Negative and zero sequence impedance of the given 3 phase transformer

APPARATUS:

- (1) 3 Phase variac
- (2) Ammeter, voltmeter, watt meter.

Range of apparatus depends on rating of transformer.

THEORY:

- (A) Positive and negative sequence impedance: Refer fig 1. (Assuming Y-Y connections. However, connections do not change value of -ve and +ve sequence impedance.
- (B) Zero sequence impedance: here neutral connection will depend upon magnitude of the impedance besides the nature of connection of windings. [Refer fig 2,3 and 4]

PROCEDURE:

FOR Z₁ (or Z₂) L. V winding for Z₀, give reduced voltage and take measurements.

CONNECTION DIAGRAM:

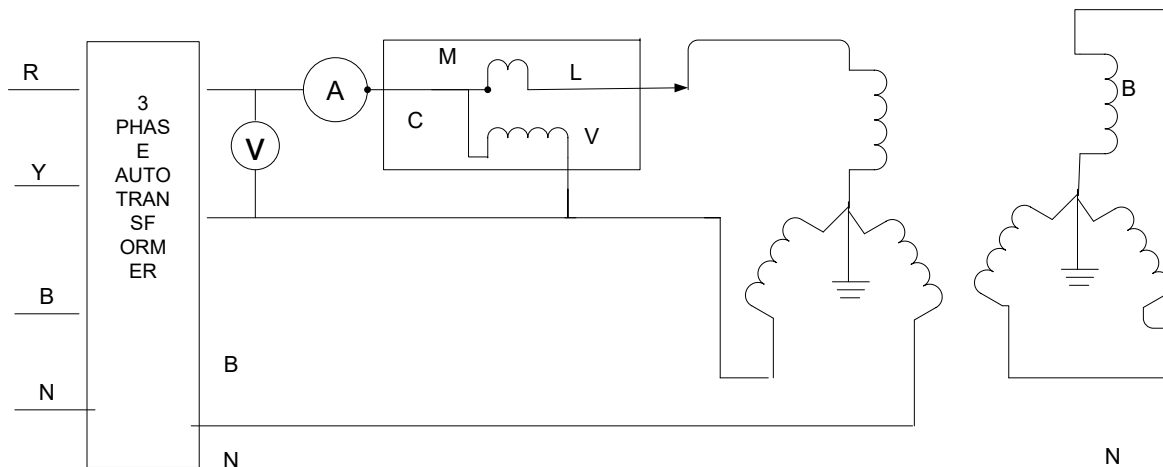


Fig: 1

For determination of Z_{01}

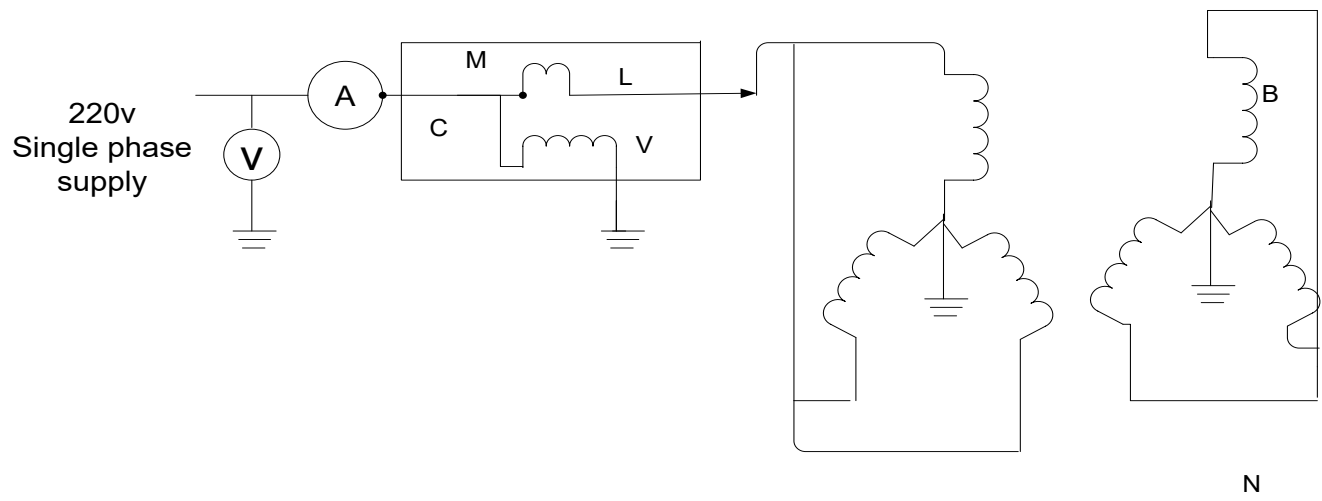


Fig: 2

For determination of Z_{02}


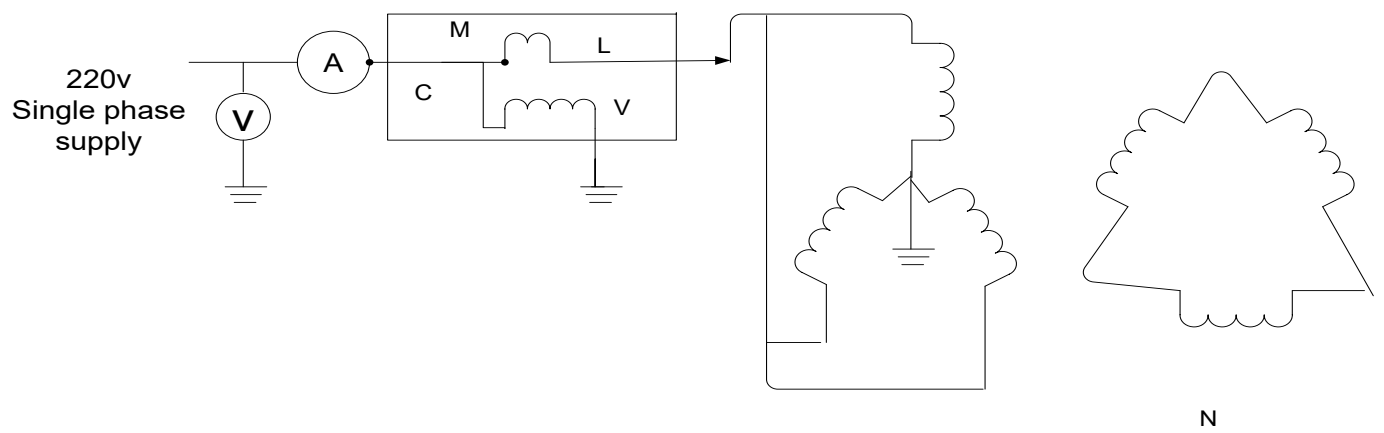


Fig: 3

For determination of Z_{03}

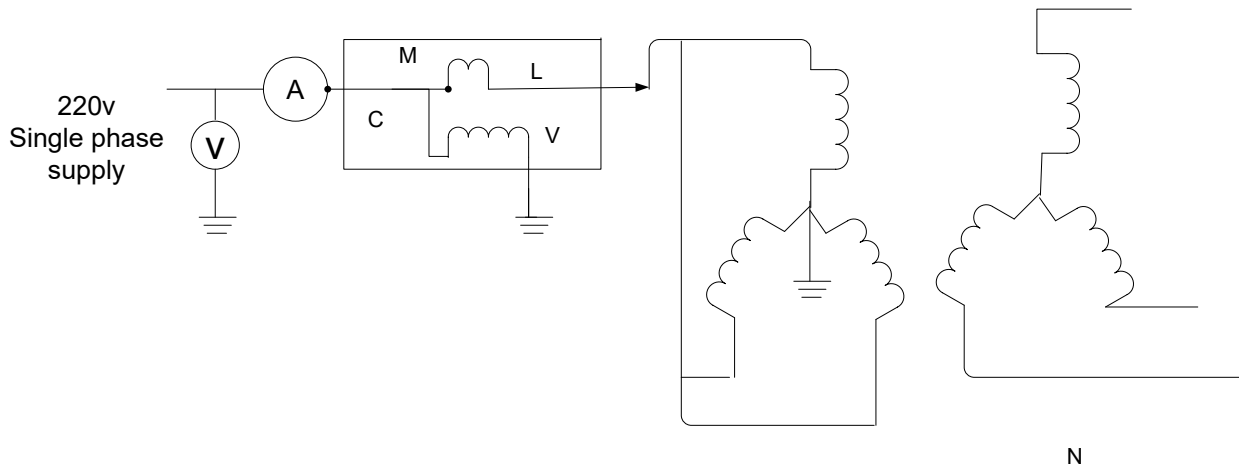

CALCULATIONS:

Z_1 = Positive sequence impedance

Z_2 = Negative sequence impedance

$$Z_1 = V/I_1; R_1 = W/I_1^2; X_1^2 = Z_1^2 - R_1^2$$

For Z_0 ,

$$I = 3 * I_0$$

$$Z_0 = E/I_0$$

$$R_0 = W/(3 * I_0)^2$$

$$X_0 = Z_0^2 - R_0^2$$

Observations:

(1) Positive / negative sequence impedance:

| Voltage(volts) | Current(amps) | Power(watts) |
|----------------|---------------|--------------|
| | | |

This is for finding Z_1 and Z_2

(2) For Z_0 i.e, zero sequence impedance:

| Voltage(volts) | Current(amps) | Power(watts) |
|----------------|---------------|--------------|
| | | |

Calculate Z_0 for fig 2, 3&4 (different connections)

RESULTS:

- (1) $Z_{01} =$ $Z_{02} =$ $Z_{03} =$
(2) $Z_1 =$ $Z_2 =$