

Experiment –

Aim : To Verify Norton's Theorem.

Apparatus :
1. Voltmeter (0-50V)
2. Ammeter (0-150 mA)
3. Resistance Network($R_1=50\Omega$, $R_2 = 150\Omega$, $R_3 = 100\Omega$)

Theory: Norton's theorem provides a mathematical technique for replacing a given network into equivalent network as viewed from two output terminals A & B. It replace the given network by a signal current source with a parallel resistance connected across two terminals A & B of a linear ,bilateral network, is given by the I_{SC} (short circuit current) and R_i the internal resistance of the network as viewed back into the open circuit. Where voltage source replaced their internal resistance and current source by infinite resistance.

Procedure :

1. The circuit is connected as shown in fig.A and reading of ammeter is noted.
2. The resistance R_3 is removed from the terminals and the ckt. redrawn as in fig.B. The terminals have become short circuited.
3. The short circuited current passing through the terminals A &B when they are short is noted down from the ammeter.
4. Next the battery is removed and the ckt. redrawn as in fig.C. When viewed from terminals A,B. & equivalent resistance of the circuit is found.
5. Using Norton's equivalent circuit find the current through R_3 and verify it.

Observations:

Result:

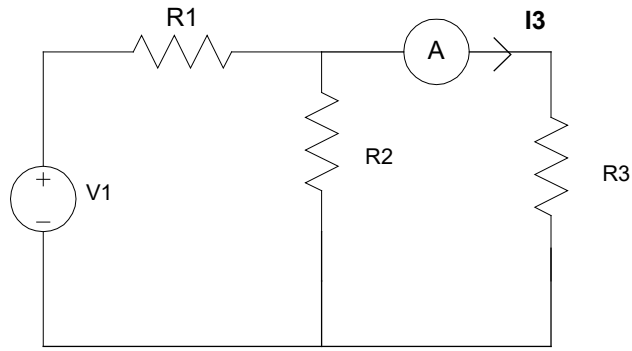


Fig.A

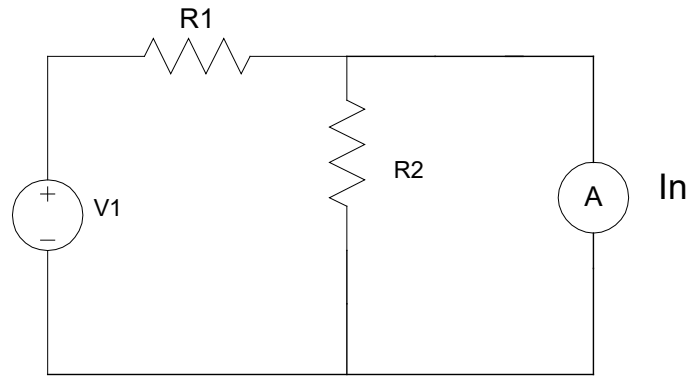


Fig.B

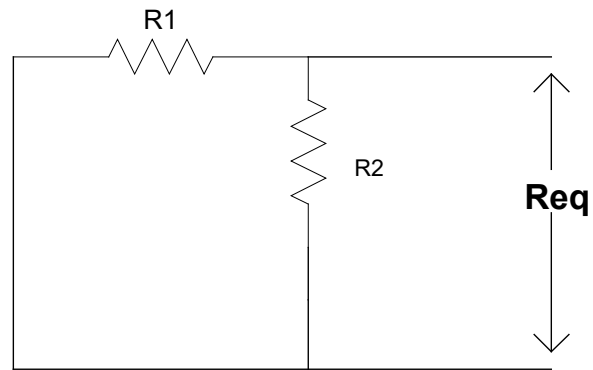


Fig.C

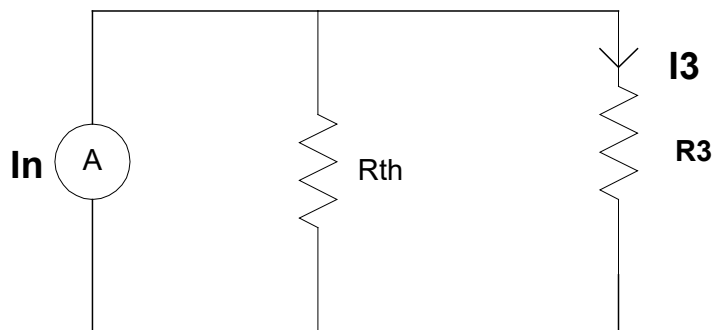


Fig.D Norton's Equivalent circuit